
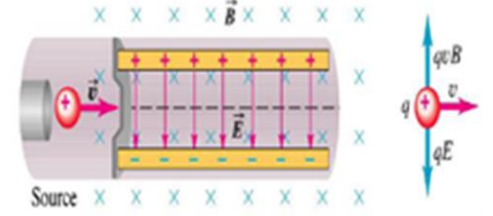
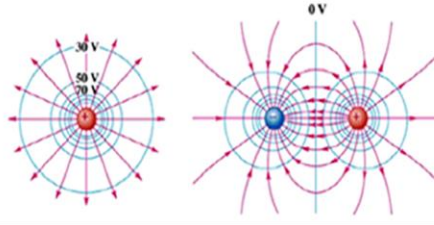


Physics-2

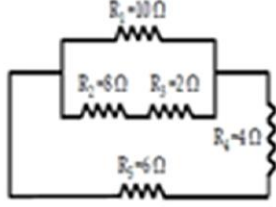

Ch-7

Resistors Connection

یوسف زویل ف

Best wishes and good Luck


00966502047005



Resistors Connection

توصيل المقاومات

التوصيل على التوالي Series Connection

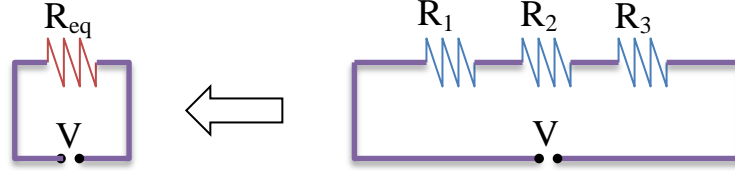

$$R_{eq} = R_1 + R_2 + R_3$$

$$I_1 = I_2 = I_3 = \frac{V}{R_{eq}}$$


التيار ثابت على التوالي

$$V_1 = I_1 R_1 \quad V_2 = I_2 R_2 \quad V_3 = I_3 R_3, \quad V = V_1 + V_2 + V_3$$

ملاحظة: في حالة توصيل عدد n من المقاومات المتساوية كل منها R على التوالي $R_{eq} = nR$

التوصيل على التوازي Parallel Connection
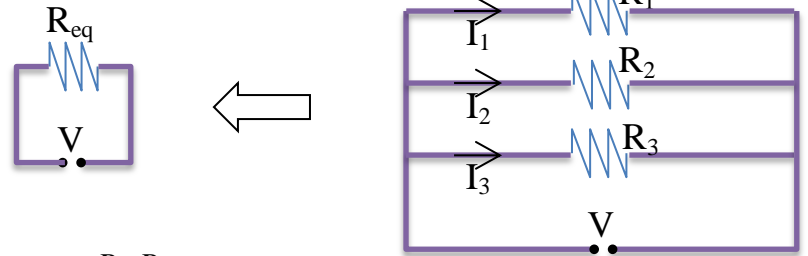
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

في حالة مقاومتي R_1, R_2

$$V_1 = V_2 = V_3 = V$$

الجهد ثابت على التوازي

$$I_1 = \frac{V_1}{R_1}$$

$$I_2 = \frac{V_2}{R_2}$$


$$I_3 = \frac{V_3}{R_3}$$

ملاحظة: في حالة توصيل عدد n من المقاومات المتساوية كل منها R على التوازي فإن: $R_{eq} = \frac{R}{n}$



Ex1: The equivalent resistance between the point a and b in the figure is:

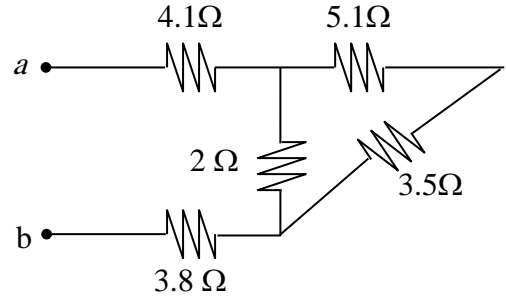- (a) 19.04Ω (b) 9.52Ω
 (c) 9.76Ω (d) 1.12Ω



Solution

نبدأ دائماً من نهاية الدائرة

$$5.1 \Omega, 3.5 \Omega \xrightarrow{\text{series}} 8.6 \Omega$$



$$8.6 \Omega // 2 \Omega \Rightarrow$$

$$\frac{1}{8.6} + \frac{1}{2} = 0.616$$

نقلب

$$1.62 \Omega$$


$$\begin{aligned} R_{eq} &= 4.1 + 1.62 + 3.8 \\ &= 9.52 \Omega \end{aligned}$$

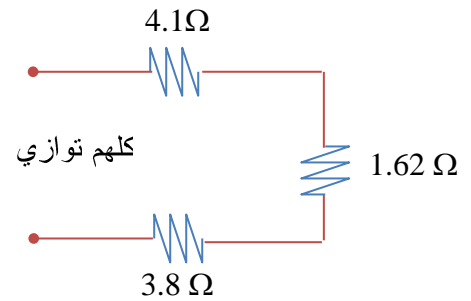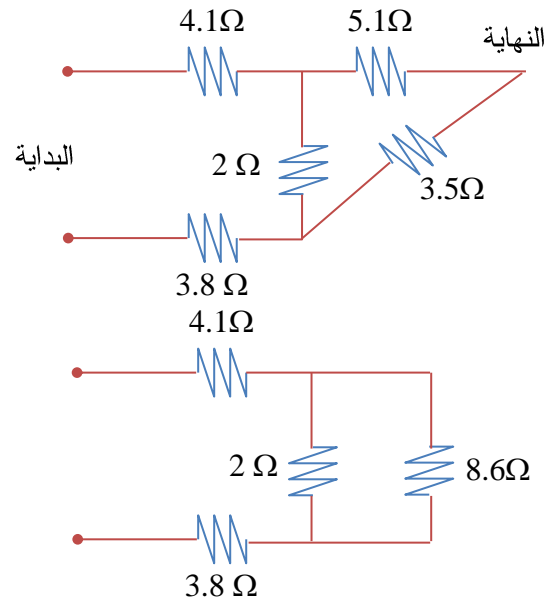



Ex2: Find the equivalent resistance between points A and B

- (a) 55Ω (b) 15Ω
 (c) 25Ω (d) 10Ω

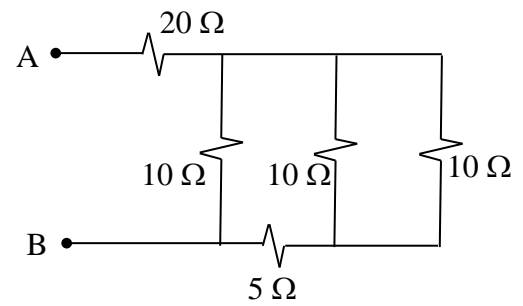





Solution

$$10 \Omega // 10 \Omega \Rightarrow \\ = \frac{1}{10} + \frac{1}{10} = \frac{1}{5} \Rightarrow 5 \Omega$$

$$5 \Omega, 5 \Omega \xrightarrow{\text{series}} 10 \Omega$$

$$10 \Omega // 10 \Omega \Rightarrow \\ = \frac{1}{10} + \frac{1}{10} = \frac{1}{5} \Rightarrow 5 \Omega$$

$$R_{eq} = 20 + 5 = 25 \Omega$$

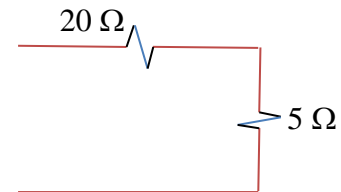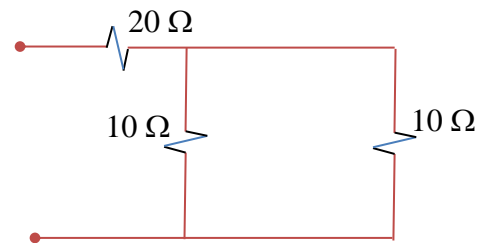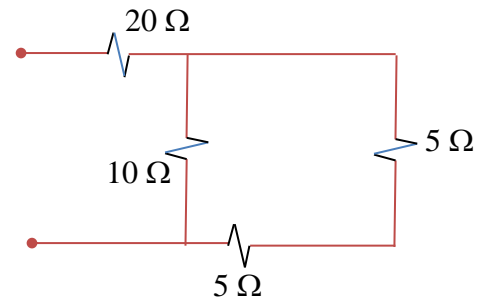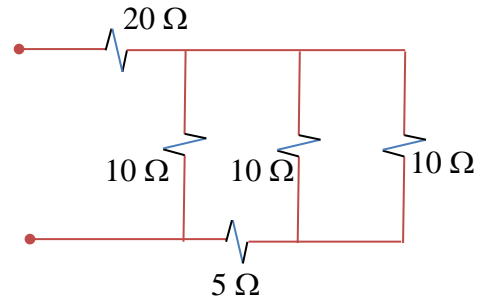


Kirchhoff's laws

(1) Kirchhoff Current Law (KCL)

عند أي عقدة (node) يكون:

مجموع التيارات الداخلة = مجموع التيارات الخارجة

العقدة تلاقى 3 أفرع على الأقل

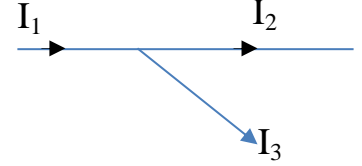


$$I_1 = I_2 + I_3$$


(2) Kirchhoff Voltage Law (KVL)

في أي مسار مغلق يكون


$$\sum V = 0$$

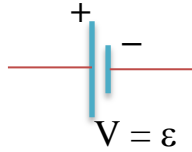

نضع الإشارة التي
يخرج منها التيار

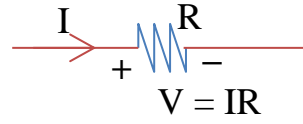

التيار يدخل من (+)
ويخرج من (-)

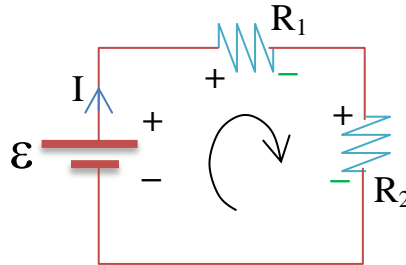

$$\varepsilon - IR_1 - IR_2 = 0$$




Ex3: Find the value of R in the circuit shown in the figure:

(a) 1Ω


(b) 5Ω

(c) 2Ω

(d) 7Ω

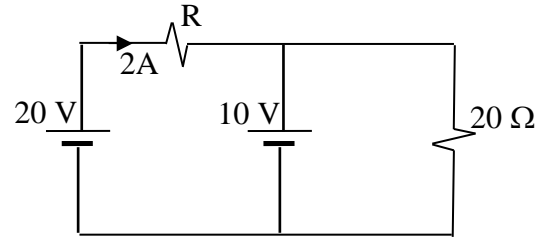

Solution

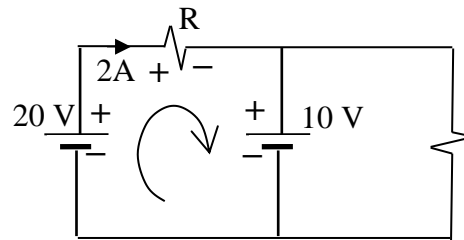

$$R = ??$$

Apply KVL

$$20 - 2R - 10 = 0$$

$$10 = 2R$$


$$\therefore R = 5 \Omega$$



Ex4: What is the power dissipated in the $3\ \Omega$ resistor shown

in the figure:

- (a) 72 W (b) 27 W
(c) 22 W (d) 36 W

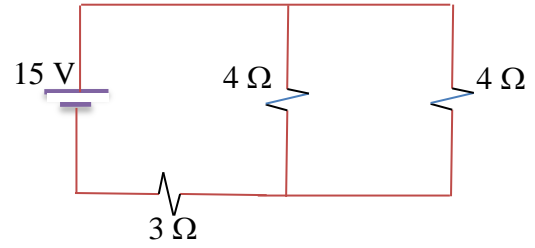


Solution

$$4\ \Omega // 4\ \Omega \Rightarrow$$

$$\frac{1}{R} = \frac{1}{4} + \frac{1}{4} = \frac{1}{2} \Rightarrow \text{نقلب } R = 2\ \Omega$$

نفرض التيار يخرج من القطب الموجب

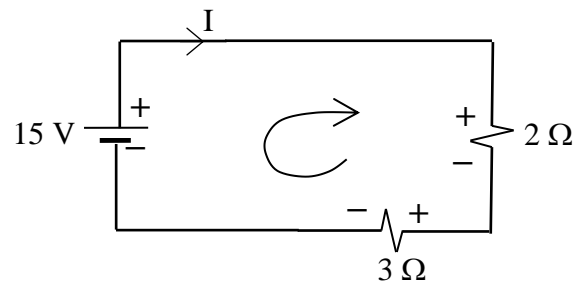

Apply KVL

$$15 - 2I - 3I = 0$$


$$15 = 5I \quad I = 3\ \text{A}$$

$$P_{3\ \Omega} = I^2 R = (3)^2 (3) = 27\ \text{W}$$




Ex5: Calculate the voltage ε of the battery shown in the figure:

- (a) 30 V (b) 40 V
(c) 10 V (d) 20 V

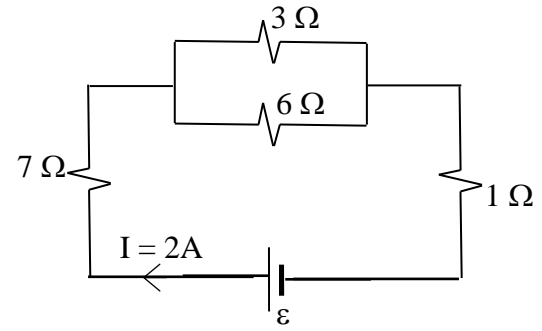

Solution
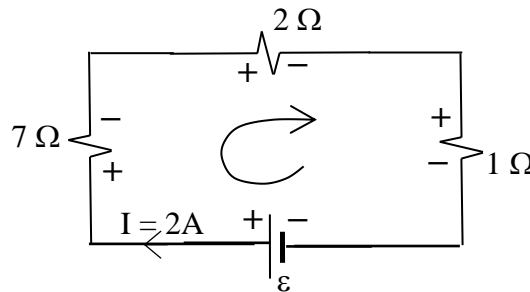
$$3 \Omega // 6 \Omega \Rightarrow \frac{1}{3} + \frac{1}{6} = \frac{1}{2} \quad \text{نقلب} \Rightarrow 2 \Omega$$



Apply KVL

$$\varepsilon - 7(2) - 2(2) - 1(2) = 0$$


$$\varepsilon = 20 \text{ V}$$



Ex6: A 12Ω resistance is connected across a battery of emf 6 V and internal resistance 0.25Ω . What potential difference will be measured across the 12Ω resistor?

- (a) 5.88 V (b) 6 V (c) 1.8 V (d) 1 V

Solution

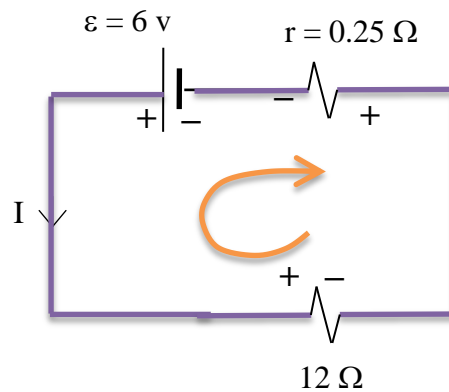

Apply KVL

$$-6 + 0.25 I + 12 I = 0$$

$$12.25 I = 6$$


$$I = \frac{6}{12.25} = 0.49 \text{ A}$$

$$V = IR = 0.49 \times 12 = 5.88 \text{ V}$$




Ex7: If $I = 1.5$ in the circuit shown. Find the potential difference $V_B - V_A$

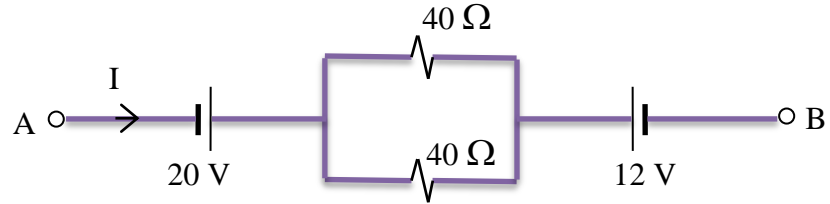- (a) -34 V (b) -40 V
(c) -10 V (d) -18 V



Solution

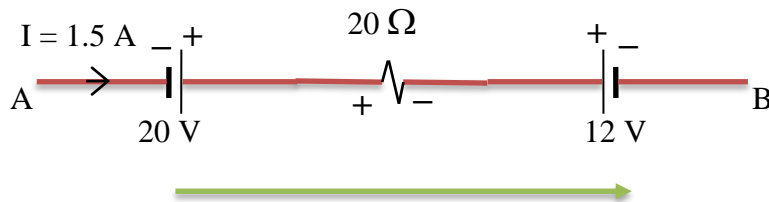

$$40 \Omega // 40 \Omega$$

$$\Rightarrow \frac{1}{40} + \frac{1}{40} = \frac{1}{20}$$

$$R_{eq} \Rightarrow 20 \Omega$$

$$V_B - V_A$$


النهاية البداية

$$\begin{aligned} V_B - V_A &= 20 - 20I - 12 \\ &= 20 - 20(1.5) - 12 \\ &= -22 \text{ V} \end{aligned}$$




Ex8: Find the current I

- (a) 8 A (b) 5 A
(c) 2 A (d) 3 A

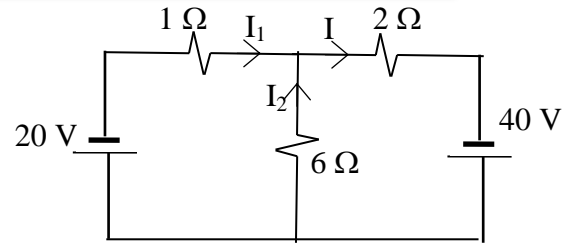


Solution

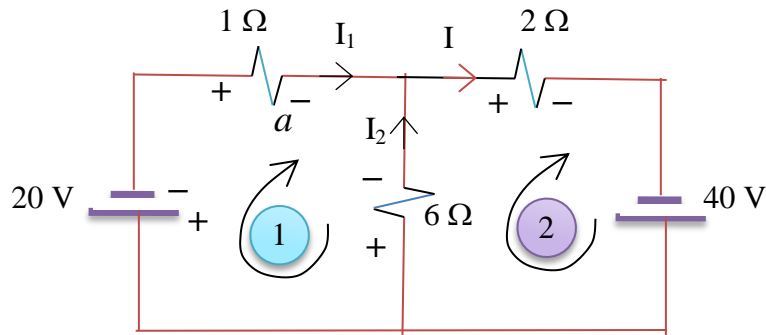

Apply KCL at node *a*

$$I_1 + I_2 = I$$


$$I_1 + I_2 - I = 0 \quad (1)$$

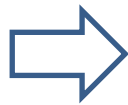

Apply KVL for loop (1)

$$-20 - (1)I_1 + 6I_2 = 0$$

$$-I_1 + 6I_2 + 0 = 20 \quad (2)$$

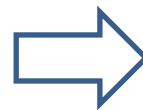

Apply KVL for loop (2)

$$-6I_2 - 2I + 40 = 0$$

$$0 - 6I_2 - 2I = -40 \quad (3)$$

Solve (1) , (2) and (3)

$$I_1 = 4 \text{ A}$$



$$I_2 = 4 \text{ A}$$

$$I = 8 \text{ A}$$



RC-Circuits

(1) Charging الشحن

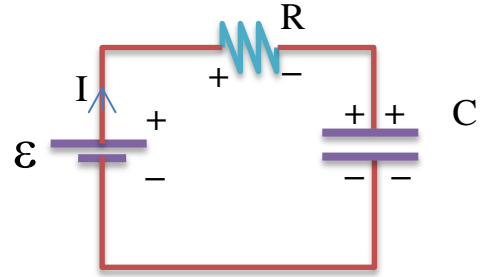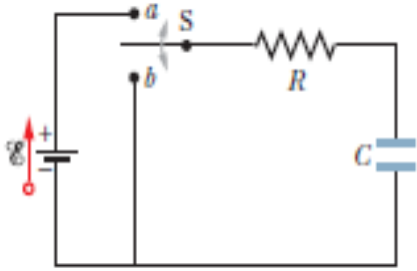


$$\varepsilon - IR - \frac{q}{C} = 0 \quad \text{من كيرشوف الثاني يكون}$$

$$q = q_0 (1 - e^{-t/\tau}) \quad , \quad V_c = \varepsilon (1 - e^{-t/\tau}) \quad , \quad i = i_0 (e^{-t/\tau})$$

$$q_0 = C \varepsilon \quad \tau = CR \quad i_0 = \frac{\varepsilon}{R}$$

| | |
|--------|--|
| q_0 | maximum charge , final charge , equilibrium charge |
| i_0 | Maximum current |
| τ | time constant |
| q | Charge on Capacitor after t second |
| V_c | potential difference on Capacitor after t second |
| i | current in Circuits after t second |

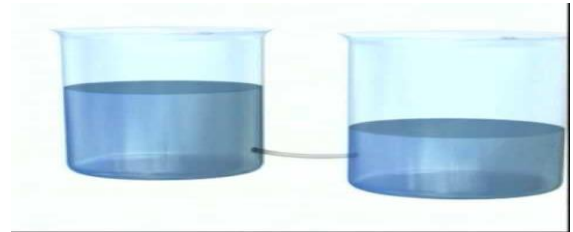



Ex10: Capacitor in an RC circuits is charged to 49% of its maximum value in 10 sec. Find the capacitance C of the circuit if $R = 5 \text{ M}\Omega$

(a) $5 \mu\text{F}$

(b) $9 \mu\text{F}$

(c) $3 \mu\text{F}$

(d) $7 \mu\text{F}$

Solution

$$q = 0.49 q_0$$


$$t = 10 \text{ S}$$

$$0.49q_0 = q_0(1 - e^{-t/\tau}) \quad \div q_0$$

$$1 - e^{-t/\tau} = 0.49$$

$$1 - 0.49 = e^{-t/\tau}$$

$$0.51 = e^{-t/\tau}$$

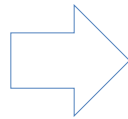


للطرفين ln

$$\ln 0.51 = \ln e^{-t/\tau}$$

$$-0.673 = -\frac{t}{\tau}$$
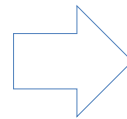
$$\tau = \frac{-10}{-0.673} = 14.85 \text{ S}$$



$$\tau = RC$$


$$C = \frac{\tau}{R} = \frac{14.85}{5 \times 10^6}$$

$$= 2.97 \times 10^{-6}$$

$$C \cong 3 \mu\text{F}$$



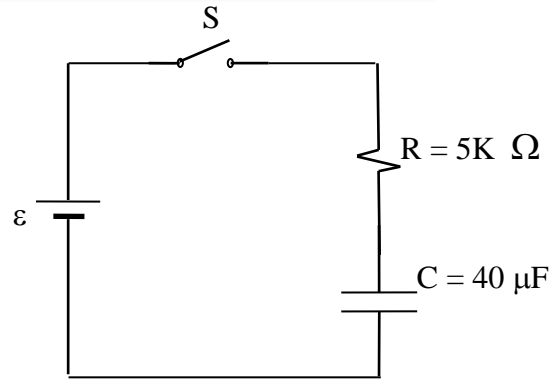Ex11: The capacitor is uncharged before the switch S is closed. the emf of the battery (ϵ) if the charge on the capacitor becomes $20 \mu\text{C}$, after $80 \mu\text{s}$ of the switch is closed.



(a) 1250 V

(b) 1250 V

(c) 1250 V

(d) 1250 V

Solution

$$R = 5 \times 10^3 \Omega, t = 80 \mu\text{s}, C = 40 \times 10^{-6} \text{ F}, q = 20 \times 10^{-6} \text{ C}$$

$$\tau = RC$$

$$= 5 \times 10^3 \times 40 \times 10^{-6}$$

$$= 0.2 \text{ S}$$

$$q = q_0 (1 - e^{-t/\tau})$$

$$20 \times 10^{-6} = q_0 (1 - e^{-\frac{80 \times 10^{-6}}{0.2}})$$

$$20 \times 10^{-6} = 3.999 \times 10^{-4} q_0$$

$$q_0 = \frac{20 \times 10^{-6}}{3.999 \times 10^{-4}} = 0.05 \text{ C}$$

$$\epsilon = \frac{q_0}{C}$$


$$= \frac{0.05}{40 \times 10^{-6}}$$

$$= 1250 \text{ V}$$



Ex12: At $t = 0$, the switch S is closed with the capacitor uncharged. If $C = 40 \mu\text{F}$ and $R = 5 \text{ K}\Omega$. How much energy is stored by the capacitor when $I = 2 \text{ mA}$?

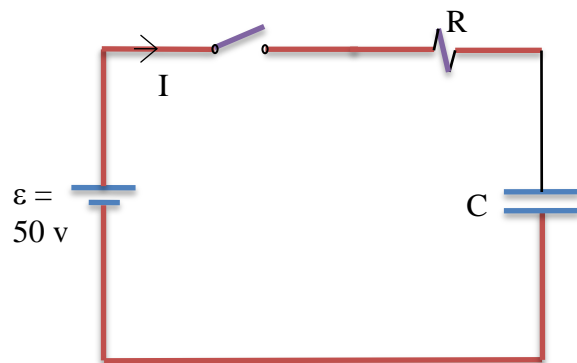- (a) $2.8 \times 10^{-2} \text{ J}$ (b) $3.6 \times 10^{-2} \text{ J}$
 (c) $3.2 \times 10^{-2} \text{ J}$ (d) $4 \times 10^{-2} \text{ J}$



Solution

$$C = 40 \times 10^{-6} \text{ F}, \quad \varepsilon = 50 \text{ V}, \quad R = 5 \times 10^3 \Omega, \quad I = 2 \text{ mA}$$

$$\tau = RC$$

$$= 5 \times 10^3 \times 40 \times 10^{-6}$$

$$= 0.2 \text{ S}$$

$$I_0 = \frac{\varepsilon}{R} = \frac{50}{5 \times 10^3}$$

$$= 0.01 \text{ A}$$



$$I = I_0 e^{-t/\tau}$$

$$2 \times 10^{-3} = 0.01 e^{-t/0.2}$$

$$e^{-t/0.2} = 0.2$$

$$\ln e^{-t/0.2} = \ln 0.2$$

$$-\frac{t}{0.2} = -1.61$$

$$t = 0.322 \text{ S}$$

$$V_C = \varepsilon (1 - e^{-t/\tau})$$

$$= 50 (1 - e^{-\frac{0.322}{0.2}})$$

$$= 40 \text{ V}$$




$$U = \frac{1}{2} C V_c^2$$

$$= \frac{1}{2} (40 \times 10^{-6}) (40)^2$$

$$= 0.032 \text{ J} = 3.2 \times 10^{-2} \text{ J}$$



(2) التفريغ Discharging

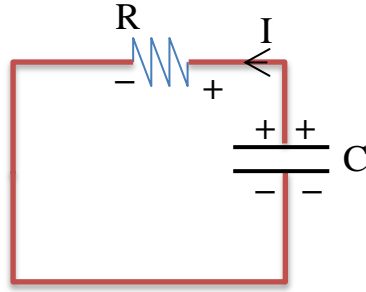

$$\tau = RC \quad , \quad q = q_0 e^{-t/\tau} \quad , \quad q_0 = C \varepsilon \quad , \quad V_c = \varepsilon e^{-t/\tau} \quad , \quad I_0 = \frac{\varepsilon}{R} \quad , \quad I = -I_0 e^{-t/\tau}$$

q_0 = initial charge

q = final charge

ε = فرق الجهد بين لوحي المكثف في بداية التفريغ

Ex13: A Capacitor of capacitance $1.8 \mu\text{F}$ is discharging through a resistance $R = 1.4 \times 10^6 \Omega$. The time at which its charge would become one-half of its initial value is

(a) 0.3 s

(b) 0.6 s

(c) 0.8 s

(d) 1.7 s


Solution

$$C = 1.8 \times 10^{-6} \text{ F} \quad , \quad R = 1.4 \times 10^6 \Omega \quad , \quad q = 0.5 q_0 \quad , \quad t = ??$$

$$\tau = RC$$

$$= 1.4 \times 10^6 \times 1.8 \times 10^{-6}$$

$$= 2.52 \text{ S}$$

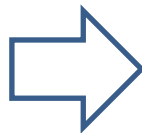

$$q_0 e^{-t/\tau} = 0.5 q_0$$

$$\ln$$

$$\ln e^{-t/2.52} = \ln 0.5$$

$$\frac{-t}{2.52} = -0.693 \Rightarrow$$

$$t = 1.75 \text{ S}$$




Ex14: A $4 \mu\text{F}$ Capacitor is charged to 24 V . Find the charge on the capacitor 4 ms after it is connected across a 200Ω resistor:

- (a) $15.5 \mu\text{C}$ (b) $2.45 \mu\text{C}$ (c) $1 \mu\text{C}$ (d) $0.324 \mu\text{C}$ (e) $0.647 \mu\text{C}$


Solution

$$V_0 = \varepsilon = 24 \text{ V} , \quad t = 4 \times 10^{-3} \text{ S} , \quad R = 200 \Omega , \quad C = 4 \times 10^{-6} \text{ F}$$
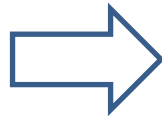
$$\begin{aligned} \tau &= R C \\ &= 200 \times 4 \times 10^{-6} \\ &= 8 \times 10^{-4} \text{ S} \end{aligned}$$


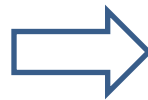
$$\begin{aligned} q_0 &= C \varepsilon \\ &= 4 \times 10^{-6} \times 24 \\ &= 96 \times 10^{-6} \text{ C} \end{aligned}$$



$$\begin{aligned} q &= q_0 e^{-t/\tau} \\ &= 96 \times 10^{-6} \times e^{-\frac{4 \times 10^{-3}}{8 \times 10^{-4}}} \\ q &= 0.647 \times 10^{-6} \text{ C} \\ &= 0.647 \mu\text{C} \end{aligned}$$